

MUTONGA BRIAN NG'ANG'A  
I39/34551/2013  
30/10/2015


## 2 BY 4 DECODER

### OBJECTIVE.

1.simulating and modelling the 2 by 4 decoder using systemc modelling language.
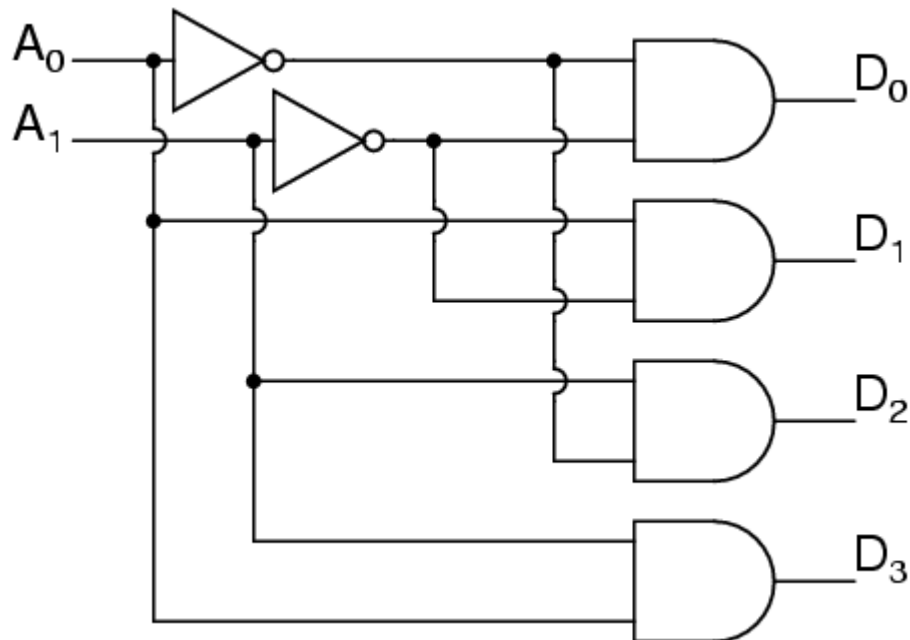
### INTRODUCTION.


A decoder is a circuit that changes a code into a set of signals. It is called a decoder because it does the reverse of encoding, this circuit takes an  $n$ -bit binary number and produces an output on one of  $2^n$  output lines .In this case this decoder takes two inputs and produces four inputs by using a combination of NOT and AND gates .By using also using truth tables to simulate all this .



**2 BY 4 DECODER SCHEMATICS**

**2 BY 4 DECODER TRUTH TABLE**

$A_1$	$A_0$	$D_3$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

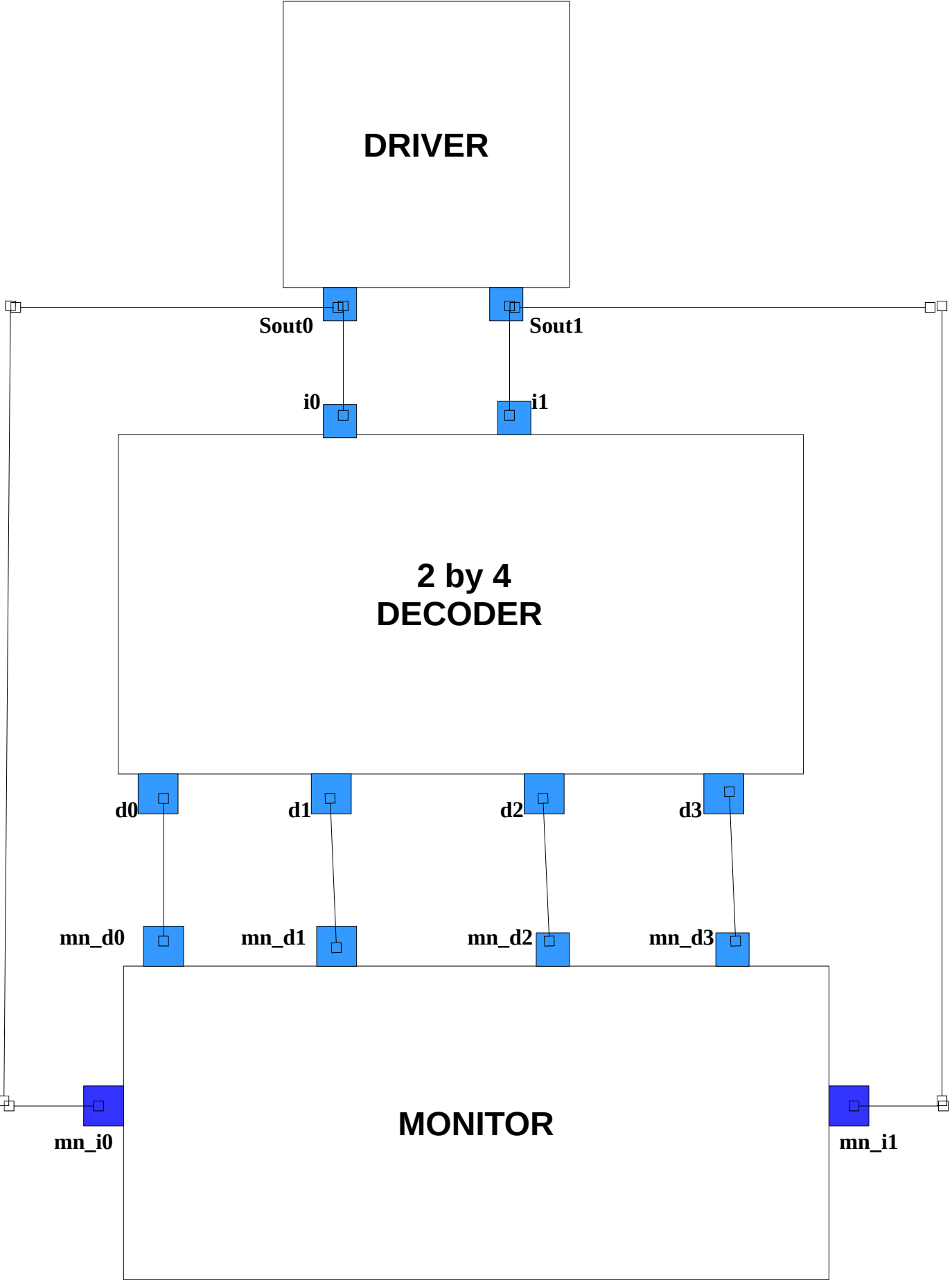

### **Driver module**

```
#ifndef DRIVER_H_
#define DRIVER_H_

#include<systemc>

SC_MODULE(driver){
    sc_out<bool> Sout0,Sout1;

    SC_CTOR(driver){
        SC_THREAD(drive);
    }

    void drive(void){
        while(1){
            Sout0=0;
            Sout1=0;
            wait(5,SC_NS);
            Sout1=1;
            wait(5,SC_NS);
            Sout0=1;
            Sout1=0;
            wait(5,SC_NS);
            Sout1=1;
            wait(5,SC_NS);
        }
    }
};

#endif
```

### **Decoder module**

```
#include<systemc.h>

SC_MODULE(decoder){
    //input and output ports
    sc_in<bool> i0,i1;
    sc_out<bool> d0,d1,d2,d3;
    //constructor: where the processes are bound to simulation kernel
    SC_CTOR(decoder){
        SC_METHOD(decode);
        sensitive<<i0<<i1; //sensitive to i0 and i1 which is the input
        //dont_initialize();
    }

    ~decoder(){
        //delete stuff :P
    }

    void decode(void){
        if (i0==0 && i1==0){
            d0=1;
```

```

d1=0;
d2=0;
d3=0; }
else if (i0==0 && i1==1){
    d1=0;
    d2=1;
    d3=0;
    d0=0;
    }
else if (i0==1 && i1==0){
    d3=0;
    d1=1;
    d2=0;
    d0=0;

}
else if (i0==1 && i1==1){
    d3=1;
    d2=0;
    d1=0;
    d0=0;
}
};

```

## **monitor.h**

```

#ifndef MONITOR_H_
#define MONITOR_H_

```

```

#include<iostream>
#include<systemc>

```

```

using namespace std;

```

```

SC_MODULE(monitor){
    sc_in<bool> mn_i0, mn_i1,mn_d0,mn_d1,mn_d2,mn_d3;

```

```

    SC_CTOR(monitor){
        SC_METHOD(monita);
        sensitive<<mn_d0<<mn_d1<<mn_d2<<mn_d3;
        dont_initialize();
    }

```

```

    void monita(void){
        cout<<"at "<<sc_time_stamp()<<" input 0 is: "<<mn_i0<<"input 1 is "<<mn_i1<<" outputs are: "<<mn_d0<<"
        and "<<mn_d1<<"and"<<mn_d2<<"and"<<mn_d3<<endl;
    }
};

```

```

#endif

```

## Decoder.cc

```
#include"decoder.h"
#include"driver.h"
#include"monitor.h"
#include<systemc>

int sc_main(int argc, char *argv[]){
//some signals for interconnections
sc_signal<bool> in_0,in_1,out0, out1,out2,out3;
//module instances
decoder dec("decoder_instance");
driver dr("driver_instance");
monitor mn("monitor_instance");
//interconnections between modules instance.port()
dr.Sout0(in_0);
dr.Sout1(in_1);
dec.i0(in_0);
dec.i1(in_1);
mn.mn_i0(in_0);
mn.mn_i1(in_1);

dec.d0(out0);
dec.d1(out1);
dec.d2(out2);
dec.d3(out3);
//monitor outputs
mn.mn_d0(out0);
mn.mn_d1(out1);
mn.mn_d2(out2);
mn.mn_d3(out3);
//create a trace file with nanosecond resolution
sc_trace_file *tf;
tf = sc_create_vcd_trace_file("timing_diagram");
tf->set_time_unit(1, SC_NS);
//trace the signals interconnecting modules
sc_trace(tf, in_0, "binary_input1"); // signals to be traced
sc_trace(tf,in_1, "binary_input2");

sc_trace(tf, out0, "input_is_zero");
sc_trace(tf, out1, "input_is_one");
sc_trace(tf, out2, "input_is_two");
sc_trace(tf, out3, "input_is_three");


//run a simulation for 50 systemc nano-seconds
if( !sc_pending_activity() )
sc_start(50,SC_NS);
//close the trace file
sc_close_vcd_trace_file(tf);
return 0;
}
```

## **Conclusion**

The modelling and simulation was successful.

## **References**

1.A SystemC Primer

J. BHASKER

Published by

Star Galaxy Publishing

015 Treeline Drive, Allentown,PA 18103

2.SystemC:

From the Ground Up

D.C. Black, J. Donovan, B. Bunton, A. Keist